
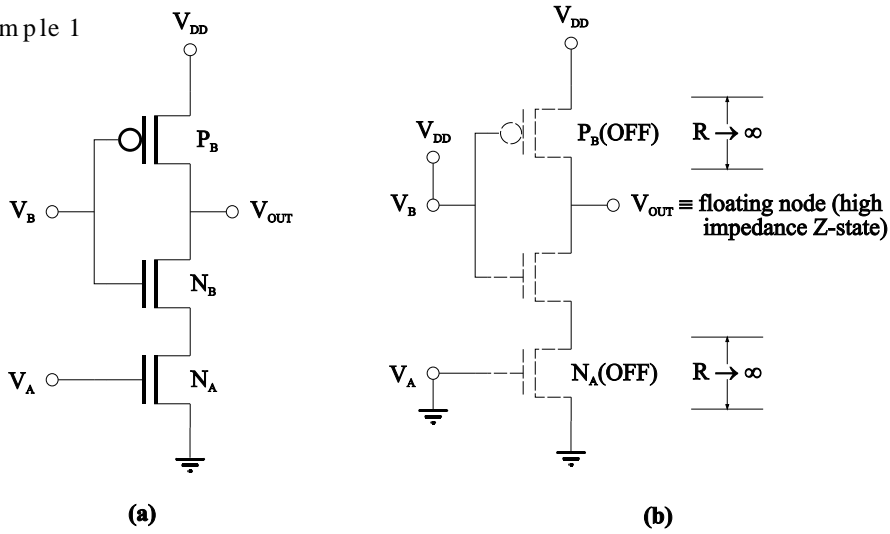


CMOS TRISTATE GATES 1

Example 1

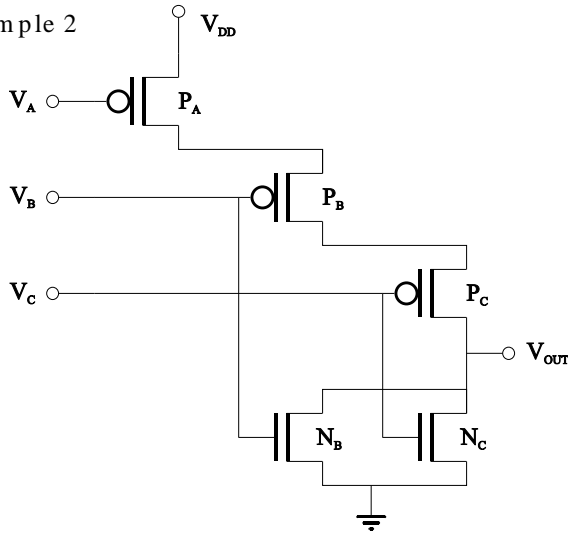

Example 2



Example 3

