

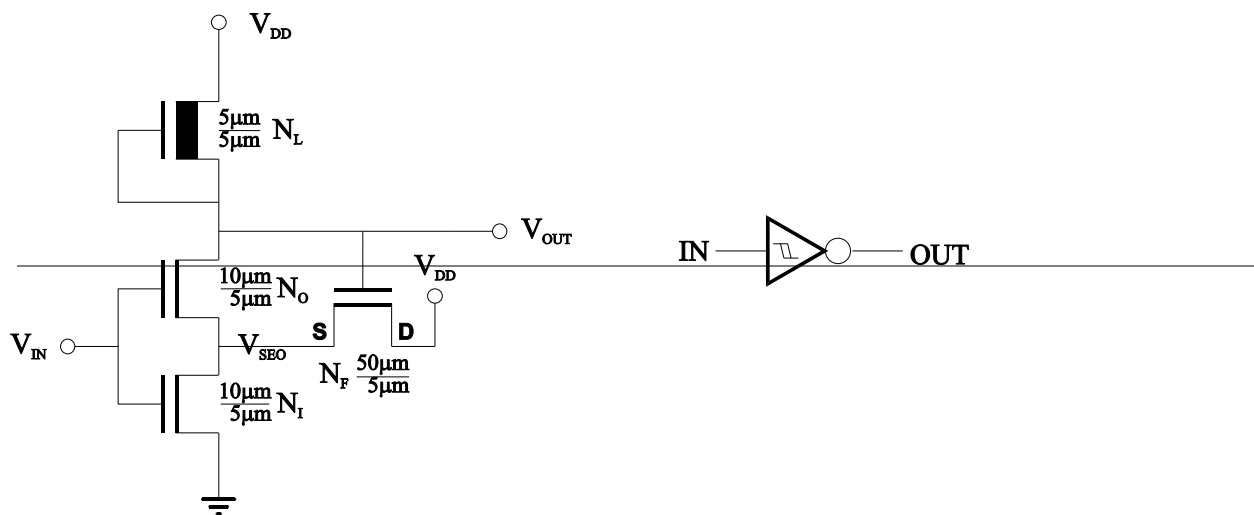


# Schmitt Trigger NMOS

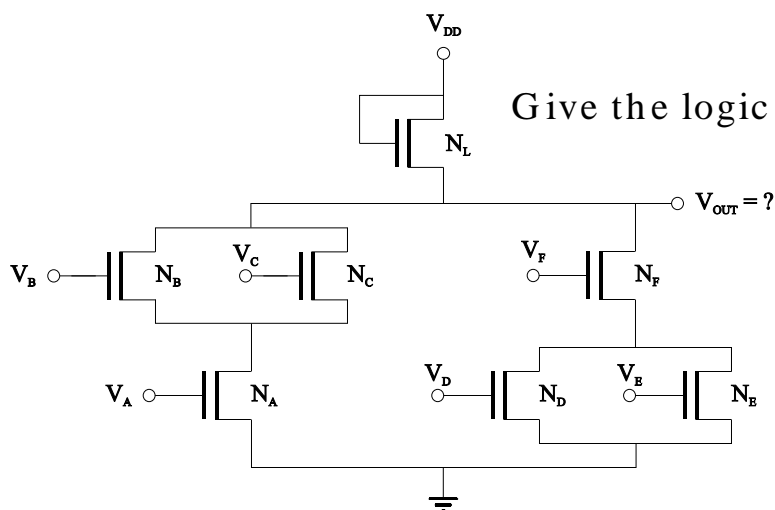

VTC has different up and down voltages

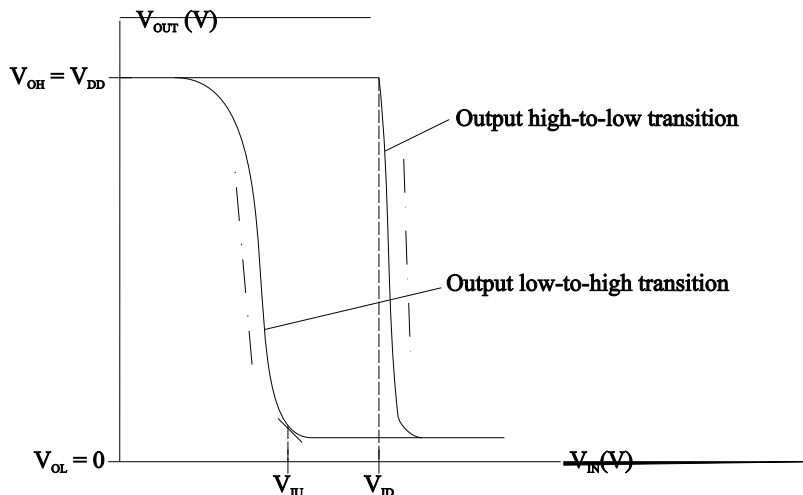

Give the logic Function