

Determine the logic function for the following circuits.

